



# **Practice Exam**

## **Design Verification**

Module ID : CX-301

### **Design Verification**

Instructor : Dr. Abid Rafique

Version 1.0

*Information contained within this document is for the sole readership of the recipient, without authorization of distribution to individuals and / or corporations without prior notification and approval.*

## Document History

The changes and versions of the document are outlined below:

Version	State / Changes	Date	Author
1.0	Initial Draft	February, 2025	Dr. Abid Rafique

# Table of Contents

<b>Document History</b>	<b>2</b>
<b>Table of Contents</b>	<b>3</b>
<b>Objectives</b>	<b>4</b>
<b>Deliverables</b>	<b>4</b>
<b>1. Micro-Circuits Verification</b>	<b>5</b>
<b>Task 1:</b>	<b>5</b>
<b>Task 2:</b>	<b>6</b>
<b>2. Mini-Circuits Design</b>	<b>7</b>

## Objectives

By the end of this practice exam, students will be able to:

- verify circuits (basic to medium difficulty level) from a given requirement specification

## Required Files

The required files for this exam can be found on the shared folder at:

```
shared_folder/CX-301-DesignVerification/Exams/Practice-Exam/
```

## Deliverables

Following are the deliverables to be uploaded on the lms:

- Verification Plan.
- Testbench


.

# 1. Micro-Circuits Verification

## Task 1:

Write a testbench to verify a circuit which takes two inputs coming from the sensors **a** and **b**. If both of them are **ON**, the output will be '**1**' otherwise it will be '**0**'. The output should be registered using a flip flop with an **enable** signal. The flip flop has an active low **rst\_n** as well.

S.No.	Signal	Number of Bits	Input/Output	Remarks
1.	clk	1	Input	
2.	rst_n	1	Input	Active Low
3.	enable	1	Input	Active High
4.	a	1	Input	
5.	b	1	Input	
6.	z	1	Output	

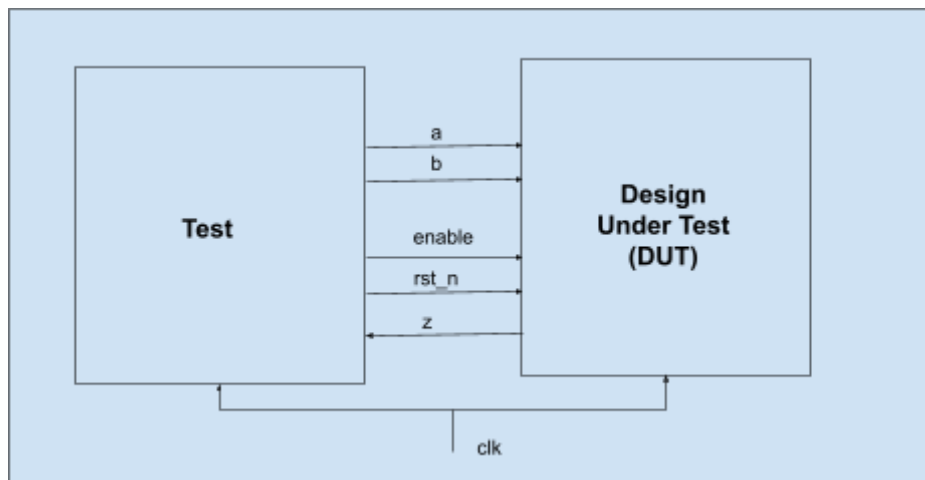

You need to perform the following tasks.

1. Write a verification plan ([see the example](#))
2. Write the testbench to test all the test cases mentioned in the verification plan

## Task 2:

Write a testbench to verify a updown-counter circuit.

- If the load signal load = 1, the 8-bit value data\_in is loaded into the counter.
- If the load signal is not active and enable signal en = 1:
  - The counter increments if the mode bit m = 0
  - The counter decrements if the mode bit m = 1.
- Active low rst\_n signals will reset the count value asynchronously.

S.No.	Signal	Number of Bits	Input/Output	Remarks
1.	clk	1	Input	synchronous to posedge
2.	rst_n	1	Input	active low reset
3.	en	1	Input	counting enable
4.	m	1	Input	counting mode
5.	load	1	Input	load data_in
6.	data_in	8	Input	the data to be loaded
7.	count	8	Output	count value


You need to perform the following tasks.

3. Write a verification plan ([see the example](#))
4. Write the testbench to test all the test cases mentioned in the verification plan
 
## 2. Mini-Circuits Design

Write a testbench to verify a Bit Serial Adder which takes two inputs 'A' and 'B' each 4-bit wide and performs addition using a multi-cycle single full-adder using following steps.

- The values will be loaded into the adder when the **load** signal is '1'.
- When the **start** signal is '1', the adder starts performing addition
- Once the addition is finished, it generates a **done** signal indicating the result is valid.



You need to perform the following tasks.

5. Write a verification plan ([see the example](#))
6. Write the testbench to test all the test cases mentioned in the verification plan

Good Luck 😊